



Computer Organization


Lab10 CPU Design(2)

IFetch, Controller, ALU,
'Single cycle' CPU



Topic

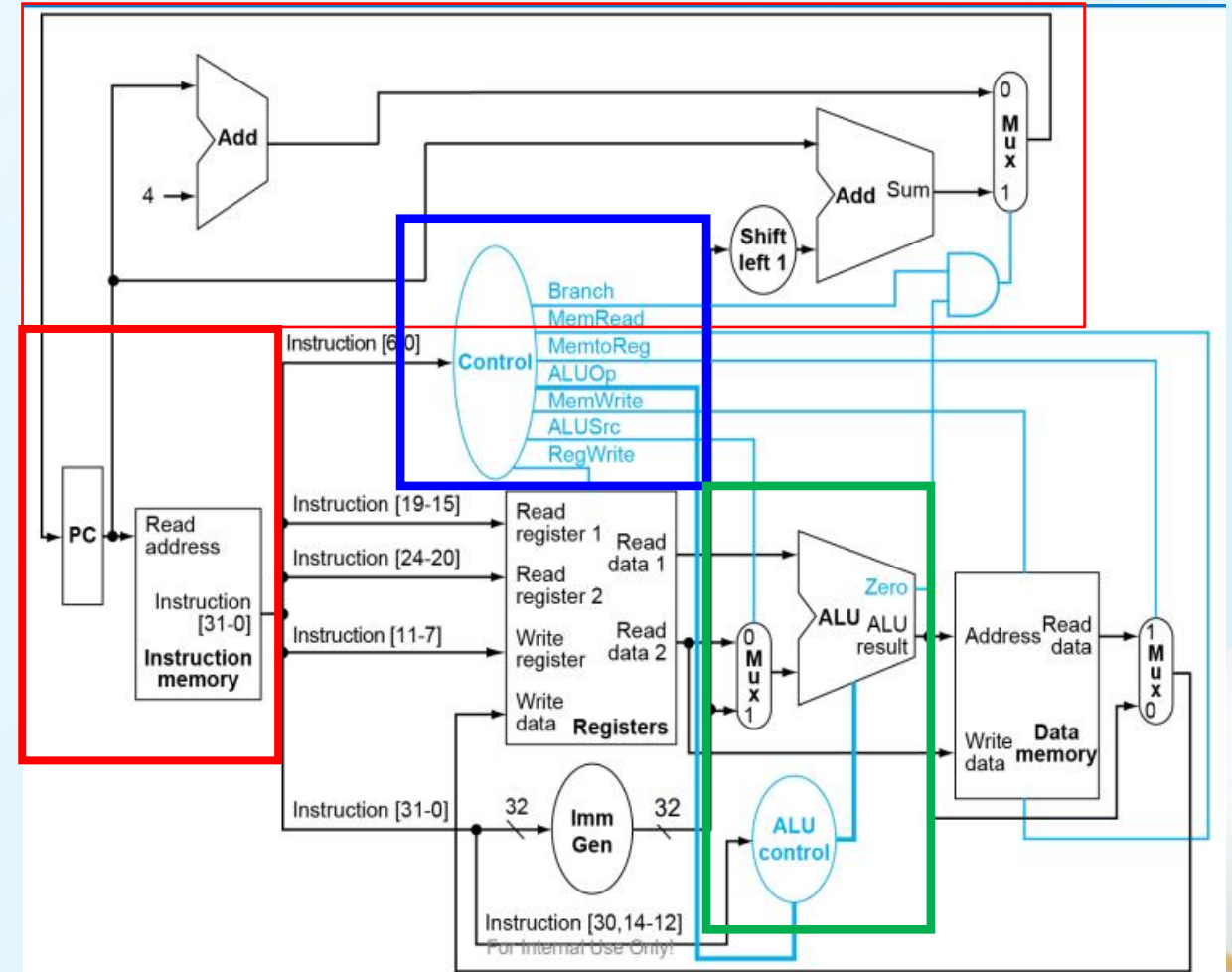- CPU Design(2)
 - Instruction Fetch(2)
 - PC + Instruction Memory
 - Instruction Analysis(2)
 - Controller
 - Instruction Execution(2)
 - ALU
 - A 'Single cycle' CPU





Instruction Fetch(2)-IFetch


- IFetch(update PC, fetch instruction according to the value of PC)
 - input: clk, branch, zero, imm32, ?
 - output: instruction
 - PC register
 - Instruction Memory(finished in lab9)
- Task 1: using verilog to describe IFetch module

```
// Structural design in verilog
module IFetch(clk,branch, zero, imm32, instruction);

    reg [/*TBD*/:0] pc;
    prgrom urom(.clka(clk), .addra(pc[15:2]), .douta(instruction));

endmodule
```

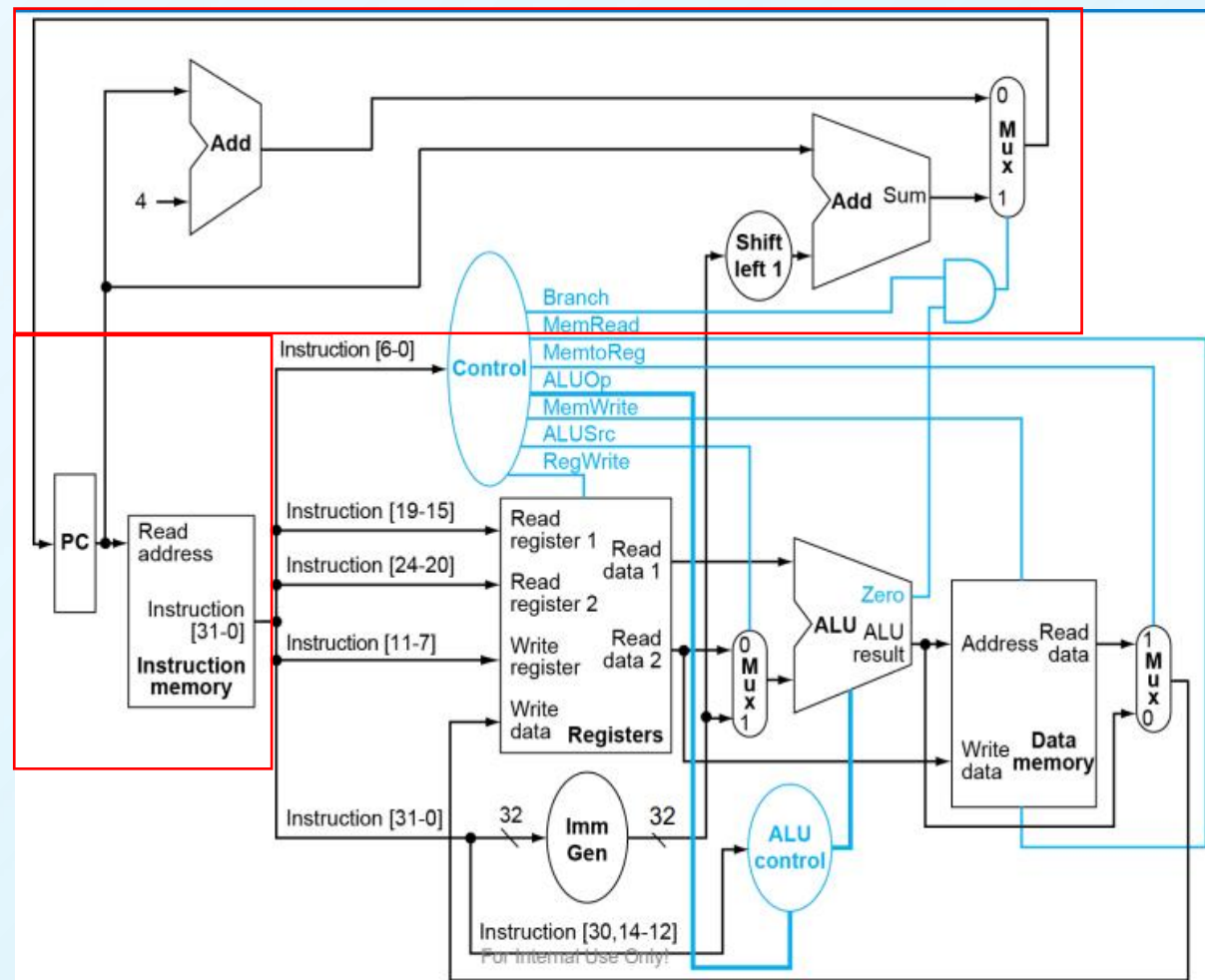Q: Why using pc[15:2] to bind with port addra of prgrom?





IFetch continued

➤ Task 2: How to initialize and update PC register

➤ How to initialize PC register?

➤ What's the initial value


➤ When to initialize

➤ How to update PC register?

➤ Where does the address come from

➤ When to update

```
//Behavior design in verilog
always@ ( /*TBD*/ ) begin
    if( /*TBD*/ )           //initialize
        pc<=/*TBD*/;
    else                    //update
        if(/*TBD*/)         //branch
            pc<=pc+imm32;
        else                //branch
            pc<=pc+4;        //Sequential execution
end
```

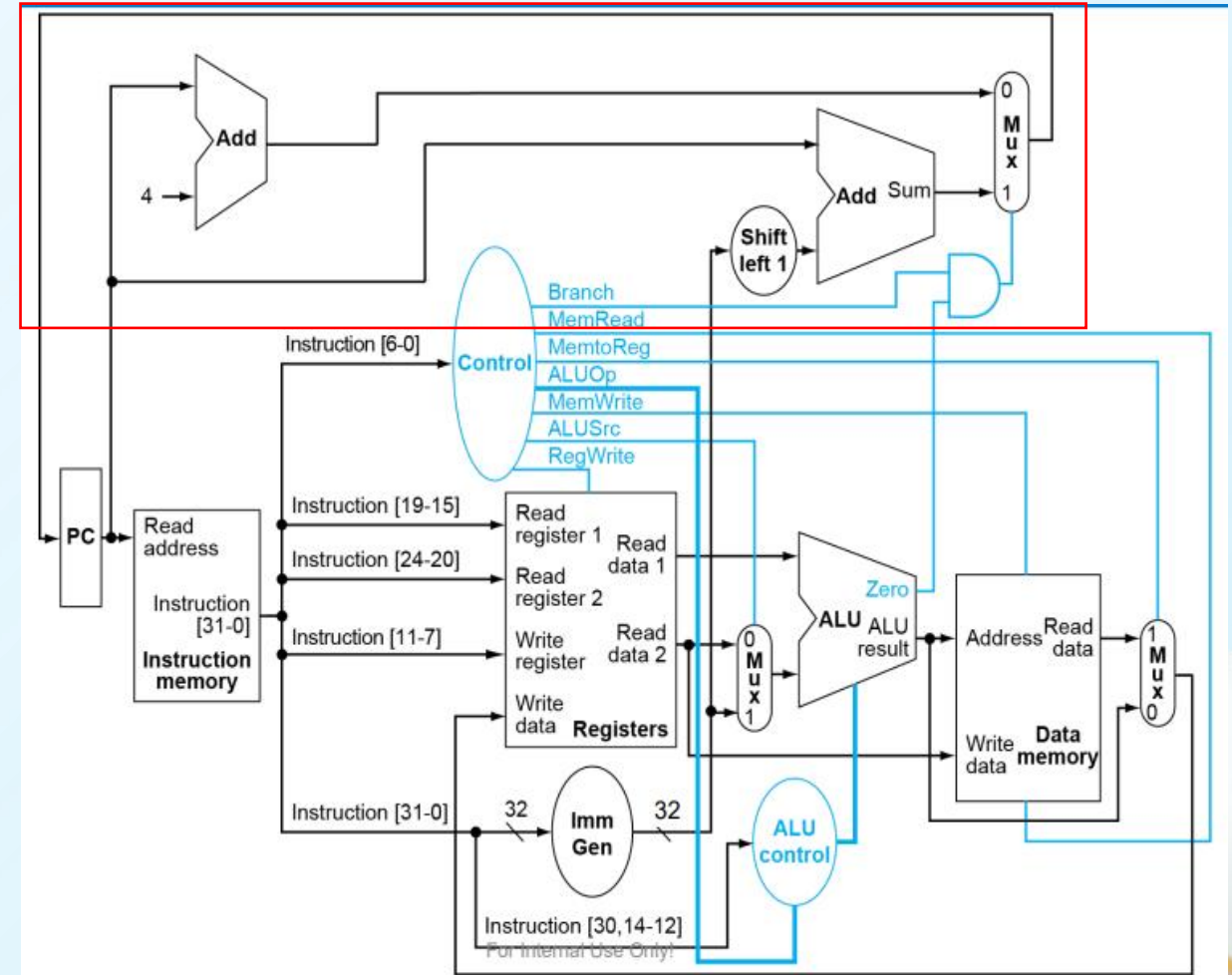



Practice1

- Implement the sub-module of a single cycle CPU: IFetch, which update PC register and fetch the instruction from the instruction memory according to the value of PC.
- Build the testbench to verify the function of IFetch.
- Tips
 - Is port list in demo ok? if not, complete it.
 - The Instruction Memory and Data Memory introduced in lab9 are different from that in Rars.

```
// Structural design in verilog
module IFetch(clk,branch, zero, imm32, instruction);

/*To be complete*/

    reg [/*TBD*/:0] pc;
    prgom urom(.clka(clk), .addra(pc[15:2]), .douta(instruction));

/*To be complete*/

//Behavior design in verilog
always@ ( /*TBD*/) begin
    if ( /*TBD*/ )                //initialize
        pc<=/*TBD*/;
    else                          //update
        if(/*TBD*/)              //branch
            pc<=pc+imm32;
        else                     //branch
            pc<=pc+4;             //Sequential execution
    end


endmodule
```






➤ **outputs**

- **Branch:** 1bit, 1'b1 while the instruction is beq, otherwise not.
- **MemRead:** 1bit, 1'b1 while need to read from Data Mem(load), otherwise not.
- **MemtoReg:** 1bit, 1'b1 while select the data read from memory to send to the Registers, otherwise not.
- **ALUOp:** 2bit, Need to be considered together with the ALU.
- **MemWrite:** 1bit, 1'b1 while need to write to Data Mem(store), otherwise not.
- **ALUSrc:** 1bit, 1'b1 while select Immediate as the operand of ALU, otherwise select the read data2 from Registers.
- **RegWrite:** 1bit, 1'b1 while need to write to Registers, otherwise not.

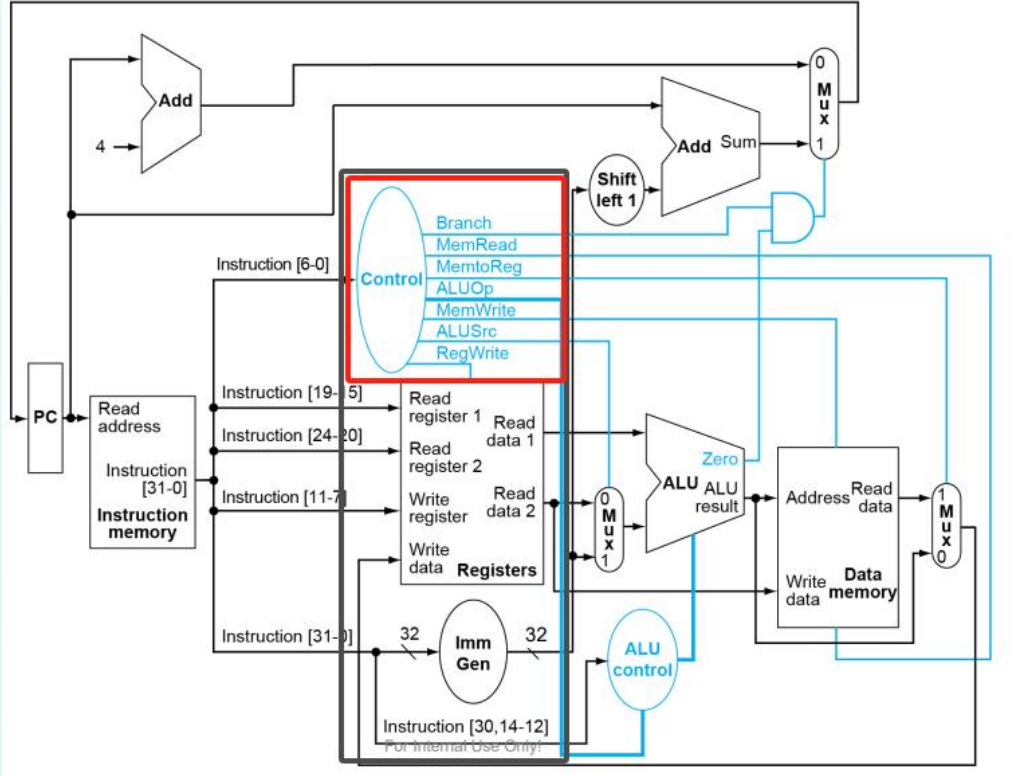

NOTES: Here is just a demo CPU which implements a subset of RISC-V : load, store, beq, add, sub, and, or.
Larger instruction sets require deeper and more analysis and implementation.



Controller continued

- **Circuit analysis:** After fetching the instruction, it is necessary to immediately align it for analysis, which does not involve storage. Therefore, a combinational logic circuit is used
- **outputs(demo1)**
 - MemRead: 1bit, 1'b1 while need to read from Data Mem(load), otherwise not.

- option1:

```
output MemRead;  
assign MemRead = (instruction[6:0]==7' h03)? 1' b1:1' b0;
```

- option2:

```
output reg MemRead;  
always @ *  
    if( instruction[6:0]==7' h03 )  
        MemRead = 1' b1;  
    else  
        MemRead = 1' b0;
```

Inst	Name	FMT	Opcode	funct3	funct7
add	ADD	R	0110011	0x0	0x00
sub	SUB	R	0110011	0x0	0x20
xor	XOR	R	0110011	0x4	0x00
or	OR	R	0110011	0x6	0x00
and	AND	R	0110011	0x7	0x00
sll	Shift Left Logical	R	0110011	0x1	0x00
srl	Shift Right Logical	R	0110011	0x5	0x00
sra	Shift Right Arith*	R	0110011	0x5	0x20
slt	Set Less Than	R	0110011	0x2	0x00
sltu	Set Less Than (U)	R	0110011	0x3	0x00
addi	ADD Immediate	I	0010011	0x0	imm[11:5]=0x00 imm[11:5]=0x00 imm[11:5]=0x20
xori	XOR Immediate	I	0010011	0x4	
ori	OR Immediate	I	0010011	0x6	
andi	AND Immediate	I	0010011	0x7	
slli	Shift Left Logical Imm	I	0010011	0x1	
srli	Shift Right Logical Imm	I	0010011	0x5	
srai	Shift Right Arith Imm	I	0010011	0x5	
slti	Set Less Than Imm	I	0010011	0x2	
sltiu	Set Less Than Imm (U)	I	0010011	0x3	
lb	Load Byte	I	0000011	0x0	
lh	Load Half	I	0000011	0x1	
lw	Load Word	I	0000011	0x2	
lbu	Load Byte (U)	I	0000011	0x4	
lhu	Load Half (U)	I	0000011	0x5	
sb	Store Byte	S	0100011	0x0	
sh	Store Half	S	0100011	0x1	
sw	Store Word	S	0100011	0x2	
beq	Branch ==	B	1100011	0x0	
bne	Branch !=	B	1100011	0x1	
blt	Branch <	B	1100011	0x4	
bge	Branch ≥	B	1100011	0x5	
bltu	Branch < (U)	B	1100011	0x6	
bgeu	Branch ≥ (U)	B	1100011	0x7	



Controller continued

➤ outputs(demo2)

➤ ALUOp: 2bit

➤ 2'b00 : load/store

➤ 2'b01: beq

➤ 2'b10: R-type

Q: What's the problem in the reference code below, fix it:

```
output [1:0] reg ALUOp;
```

```
always @ *
```

```
case( instruction[6:0])
```

```
7'h03,7'h23: ALUOp = 2'b00;
```

```
7'h33,7'h63: ALUOp = 2'b01;
```

```
default: ALUOp = 2'b10;
```

```
endcase
```

Instruction opcode	ALUOp	Operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
ld	00	load doubleword	XXXXXXX	XXX	add	0010
sd	00	store doubleword	XXXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001

Inst	Name	FMT	Opcode	funct3	funct7
add	ADD	R	0110011	0x0	0x00
sub	SUB	R	0110011	0x0	0x20
xor	XOR	R	0110011	0x4	0x00
or	OR	R	0110011	0x6	0x00
and	AND	R	0110011	0x7	0x00
sll	Shift Left Logical	R	0110011	0x1	0x00
srl	Shift Right Logical	R	0110011	0x5	0x00
sra	Shift Right Arith*	R	0110011	0x5	0x20
slt	Set Less Than	R	0110011	0x2	0x00
sltu	Set Less Than (U)	R	0110011	0x3	0x00
addi	ADD Immediate	I	0010011	0x0	imm[11:5]=0x00 imm[11:5]=0x00 imm[11:5]=0x20
xori	XOR Immediate	I	0010011	0x4	
ori	OR Immediate	I	0010011	0x6	
andi	AND Immediate	I	0010011	0x7	
slli	Shift Left Logical Imm	I	0010011	0x1	
srli	Shift Right Logical Imm	I	0010011	0x5	
srai	Shift Right Arith Imm	I	0010011	0x5	
slti	Set Less Than Imm	I	0010011	0x2	
sltiu	Set Less Than Imm (U)	I	0010011	0x3	
lb	Load Byte	I	0000011	0x0	
lh	Load Half	I	0000011	0x1	
lw	Load Word	I	0000011	0x2	
lbu	Load Byte (U)	I	0000011	0x4	
lhu	Load Half (U)	I	0000011	0x5	
sb	Store Byte	S	0100011	0x0	
sh	Store Half	S	0100011	0x1	
sw	Store Word	S	0100011	0x2	
beq	Branch ==	B	1100011	0x0	
bne	Branch !=	B	1100011	0x1	
blt	Branch <	B	1100011	0x4	
bge	Branch ≥	B	1100011	0x5	
bltu	Branch < (U)	B	1100011	0x6	
bgeu	Branch ≥ (U)	B	1100011	0x7	



Practice2

- Implement the sub-module of CPU: Controller
 - The controller is expected to support the specified set (add, sub, and, or, lw, sw, beq), demos on the courseware can serve as a reference.
 - Build the testbench to verify the function of Controller(here is a reference):

```
lw [0000a083]: Branch[0], ALUOp[0], ALUsrc[1], MemRead[1], MemWrite[0], MemtoReg[1], RegWrite[1]
add[001080b3]: Branch[0], ALUOp[2], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[1]
sw [00102423]: Branch[0], ALUOp[0], ALUsrc[1], MemRead[0], MemWrite[1], MemtoReg[0], RegWrite[0]
beq[fe1008e3]: Branch[1], ALUOp[1], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[0]
bne[00101663]: Branch[0], ALUOp[1], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[0]
sub[403000b3]: Branch[0], ALUOp[2], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[1]
and[0041f133]: Branch[0], ALUOp[2], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[1]
or [005261b3]: Branch[0], ALUOp[2], ALUsrc[0], MemRead[0], MemWrite[0], MemtoReg[0], RegWrite[1]
```

- it's strongly recommended to think about that which input and output ports, as well as internal processing logic, the controller needs to add if it needs to support instructions other than the specified set (add, sub, and, or, lw, sw, beq) in RISC-V32I.



- inputs:

- ✓ datas from Decoder (**ReadData1**, **ReadData2**, **imm32**), all three have a 32-bit bit width

- ✓ **ALUOp: 2bit**

Q: Are funct3 or funct7 needed here?

- outputs:

- ✓ **ALUResult:** 32bit, the result of calculation in ALU

- ✓ **zero:** 1 bit, 1' b1 while AULResult is zero, otherwise not

➤ functions:

- ✓ 1. generate **ALUControl (4bit)**
- ✓ 2. select **operand2** from ReadData2 and imm32
- ✓ 3. calculate on ReadData1 and operand2 according to the **ALUControl**, assign the calculation result to **ALUResult**
- ✓ 4. generate **zero** according to ALUResult





ALU continued

ALU:

- **Circuit analysis:** After get the control signals from controller and datas from Decoder, it is necessary to immediately calculate the result which does not involve storage. Therefore, a combinational logic circuit is used.
- Implements (Demo for load, store, beq, add, sub, and, or):
 - ✓ 1. generate **ALUControl**

```
reg [3:0] ALUControl;
```

```
always @ *  
    case( ALUOp)  
        2'b00,2'b01: ALUControl = { ALUOp, 2'b10};  
        2'b10:  
            //complete code here  
    endcase
```

Instruction opcode	ALUOp	Operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
ld	00	load doubleword	XXXXXXX	XXX	add	0010
sd	00	store doubleword	XXXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001

ALU:

- Implements(Demo):
 - ✓ 3. calculate on ReadData1 and operand2 according to the ALUControl, assign the calculation result to **ALUResult**

```
output reg [31:0] ALUResult;
```

```
//operand2 is the 2nd operand for the calculation  
always @ *  
    case( ALUControl)  
        4'b0010: ALUResult= ReadData1 + operand2;  
        4'b0110: ALUResult= ReadData1 - operand2;  
        //complete code here  
    endcase
```



 

➤ Demos:

- ✓ 2. select **operand2** from ReadData2 and imm32

```
assign operand2 = (ALUSrc==1)? ReadData2 : imm32;
```

- ✓ 4. generate **zero** according to ALUResult

```
assign zero = (ALUResult==1)? 1'b1: 1'b0;
```






Practice3

- Implement the sub-module of CPU: ALU
 - The ALU is expected to support the specified set (add, sub, and, or, lw, sw, beq), demos on the courseware can serve as a reference.
 - Build the testbench to verify the function of ALU
 - TIPS: It's suggested that integrating controller and alu into one module for testing after finish the function verification on Controller.
- it's strongly recommended to think about that which input and output ports, as well as internal processing logic, the ALU needs to add if it needs to support instructions other than the specified set (add, sub, and, or, lw, sw, beq) in RISC-V32I.

A 'single cycle' CPU

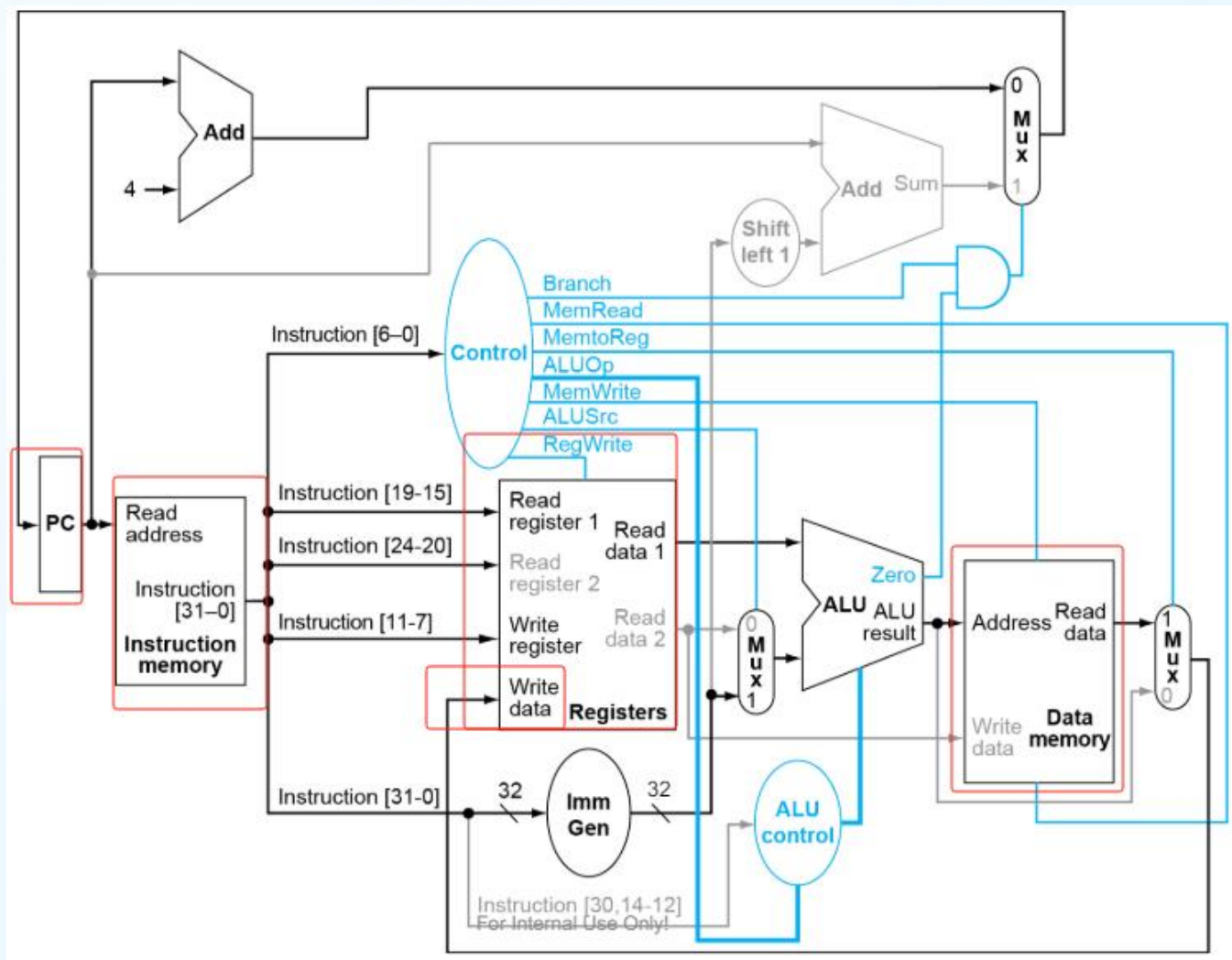

Q1. Does it **take time** for signals to be processed and transmitted within the module, as well as between modules?

Q2. Which sub modules within CPU **need the trigger from the clock**? When does the following event occur in a clock cycle?

- 1-1) **IFetch: update** the value of PC register
- 1-2) **IFetch: fetch** the instruction according to the value of PC

- 2-1-1) **Controller: generate the control signals**
- 2-2-1) **Decoder: get the value of register(s)**
- 2-2-2) **Decoder: generate the extended immediate**

- 3-1) **ALU: get the operands**
- 3-2) **ALU: generate the calculation result**

- 4-1) **Dmemory: get the address**(from ALU) and **data**(from Decoder)
- 4-2) **Dmemory: read out the data**

- 5-1) **Decoder: write back the data**



-
- The diagram illustrates the MIPS architecture with the following components and connections:
- PC (Program Counter):** Provides the address to Instruction Memory.
 - Instruction Memory:** Receives the PC address and outputs instruction fields: [31:0], [19:15], [24:20], [11:7], and [30:14:12].
 - Control:** Receives instruction fields [6:0] and [30:14:12] to generate control signals: Branch, MemRead, MemtoReg, ALUOp, MemWrite, ALUSrc, and RegWrite.
 - Registers:**
 - Read registers:** Receive instruction fields [19:15] and [24:20] to output Read data 1 and Read data 2.
 - Write register:** Receives instruction field [11:7] to output Write data.
 - Imm Gen (Immediate Generator):** Takes instruction field [31:0] and outputs a 32-bit immediate value.
 - ALU (Arithmetic Logic Unit):**
 - Inputs: Read data 1, Read data 2, and the 32-bit immediate from Imm Gen.
 - Control: Receives ALUOp and ALUSrc signals.
 - Outputs: ALU result and Zero flag.
 - Mux 1 (Multiplexer 1):** Selects between Read data 1, Read data 2, and the ALU result based on the MemtoReg control signal to produce the ALU Sum.
 - Add (Adder):** Adds the PC value and the ALU Sum to produce the next PC value.
 - Mux 0 (Multiplexer 0):** Selects between the ALU result and the ALU Sum based on the MemWrite control signal to produce the Data memory Address.
 - Data Memory:** Receives the Address and outputs Read data and Write data based on MemRead and MemWrite control signals.

```

module CPUv1( input clk, rst );
    wire [31:0] inst, imm32;
    wire branch,zero;

    IFetch uIF( .clk(clk), .rst(rst), .branch(branch), .zero(zero), );

    Controller uCtrl(.inst(inst), .Branch(branch), );

    Decoder uDecd( .clk(clk), .rst(rst), .regWrite(RegWrite), );

    ALU uALU( .rs1D(rs1Data), .rs2D(rs2Data), .imm32(imm32), );

    DMem uDMem( .clk(clk), .addr(alu_out), .din(rs2Data), );

endmodule

```




Test a 'single cycle' CPU(1)

Q1. How to test the CPU ?

how to determine the program, the data, how to check the result?

Solution 1: Simulation

```
module tb_cpu();

CPUv1 uCPU(.clk(clk), .rst(rst));
initial begin
    clk = 1'b0;
    forever #5 clk = ~clk;
end


initial begin
    rst = 1'b0;
    #20 rst = 1'b1;
    #180 $finish;
end
endmodule
```

Tips: Tools in **labs/Tools** of blackboard sit are suggested to use to generate testcase.

```
test_instr.asm
1 .data 1
2 idata: .word 0x12345678
3 .text
4 main:
5 beq x0,x1,here
6 add x0,x0,x0
7 xor x0,x0,x0
8 la t0,idata
9 lb x1,(t0)
```

```
test_instr_text0 - 记事本
文件(F) 编辑(E) 格式(O) 查
00100c63
00000033
00004033
00002297
ff428293
00028083
```

2	Code	Basic	Source
	0x00100c63	beq x0,x1,0x00000018	5: beq x0,x1,here
	0x00000033	add x0,x0,x0	6: add x0,x0,x0
	0x00004033	xor x0,x0,x0	7: xor x0,x0,x0
	0x00002297	auipc x5,2	8: la t0,idata
	0xff428293	addi x5,x5,0xffffffff4	
	0x00028083	lb x1,0(x5)	9: lb x1,(t0)

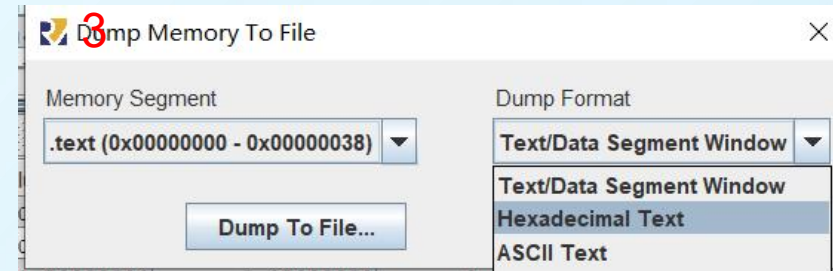

```
rars2coe.exe test_instr_text0.txt prgrom32.coe
```

Tips: Method about how to generate coe file could be find in **labs/lab9**

名称	类型
prgrom32	COE 文件
rars2coe	应用程序
test_instr_text0	文本文档




Test a 'single cycle' CPU(1) continued

Solution 1: Simulation

```
module tb_cpu();

CPUv1 uCPU(.clk(clk), .rst(rst));
initial begin
    clk = 1'b0;
    forever #5 clk = ~clk;
end

 initial begin
    rst = 1'b0;
    #20 rst = 1'b1;
    #180 $finish;
end
endmodule
```



The signals in testbench are not sufficient to determine whether the CPU is functioning properly.

Internal signals of the CPU could be added to the waveform to assist in the judgment.

The screenshot shows the simulation tool interface. The 'Scope' window on the left lists the design hierarchy: tb_cpu, uCPU, uIF, uCtrl, uDecd, and uALU. The 'Objects' window on the right shows the internal signals of the selected uCtrl module: inst[31:0], Branch, MemRead, MemtoReg, MemWrite, and ALUSrc. A context menu is open over the MemWrite signal, showing options 'Add to Wave Window' and 'Log to Wave Database'.

Tips: First, select the **submodule** to be observed in the **scope** window, and then select the **signal** to be observed in the submodule in the **object** window. **Right click on these signals**, select “**Add to wave Window**”, and **perform the simulation again**.